

# Canadian Amateur Radio Operator Guide

## Advanced

### Contents

<b>Keywords</b>	<b>1</b>
<b>1 Advanced Theory</b>	<b>1</b>
1.1 RC circuits . . . . .	1
1.1.1 Time constant . . . . .	1
1.2 RL circuits . . . . .	1
1.2.1 Time constant . . . . .	1
1.2.2 Back EMF . . . . .	1
<b>2 Advanced Components and Circuits</b>	<b>2</b>
<b>3 Measurements</b>	<b>2</b>
<b>4 Power Supplies</b>	<b>2</b>
<b>5 Transmitters, Modulation, and Processing</b>	<b>2</b>
<b>6 Receivers</b>	<b>2</b>
<b>7 Feedlines - Matching and Antenna Systems</b>	<b>2</b>

## Keywords

**farad** The unit of capacitance (symbol:  $F$ ), 1 farad is the capacitance of a capacitor that has a charge of 1 coulomb when applied voltage drop of 1 volt.

**henry** The unit of inductance (symbol:  $H$ ), 1 henry is the amount of inductance that causes a voltage of one volt, when the current is changing at a rate of one ampere per second.

**RC circuit** A resistor–capacitor circuit (RC circuit), or RC filter or RC network, is an electric circuit composed of resistors and capacitors driven by a voltage or current source. A first order RC circuit is composed of one resistor and one capacitor and is the simplest type of RC circuit.

**RL circuit** A resistor–inductor circuit (RL circuit), or RL filter or RL network, is an electric circuit composed of resistors and inductors driven by a voltage or current source. A first-order RL circuit is composed of one resistor and one inductor and is the simplest type of RL circuit.

## 1 Advanced Theory

### 1.1 RC circuits

#### 1.1.1 Time constant

The time constant of an RC circuit (in seconds), is equal to the product of the circuit resistance (in ohms) and the circuit capacitance (in farads).

$$\tau = R \cdot C$$

For example:

$$6s = 2\Omega \cdot 3F$$

It is the time required to:

- **charge** the capacitor from an initial charge voltage of zero to approximately **63.2%** of the value of an applied DC **voltage**, or
- **discharge** the capacitor to approximately **36.8%** of its initial charge **voltage**.

### 1.2 RL circuits

#### 1.2.1 Time constant

The time constant of an RL circuit (in seconds), is equal to the circuit inductance (in henries) divided by the circuit resistance (in ohms).

$$\tau = L/R$$

For example:

$$3s = 6H/2\Omega$$

It is the time required to:

- **build** the current in the **circuit** up to **63.2%** of its maximum value.

#### 1.2.2 Back EMF

Back EMF or ‘counter electromotive force’ is the voltage induced by changing current in an inductor. It is the force opposing changes in current through inductors. **Back EMF is A voltage that opposes the applied EMF.**

- 2 Advanced Components and Circuits
- 3 Measurements
- 4 Power Supplies
- 5 Transmitters, Modulation, and Processing
- 6 Receivers
- 7 Feedlines - Matching and Antenna Systems